

SIGNALS AND SYSTEMS - EE1205 LAB REPORT

FM TRANSMITTER

By - Nimal Sreekumar EE23BTECH11044.

Aim:

The aim of this experiment is to build a simple FM transmitter circuit and investigate its functionality.

Materials required:


- 1) Microphone
- 2) capacitors ($0.001\text{ }\mu\text{F}$ and $(2 \times) 10\text{ pF}$)
- 3) Resistor ($4.7\text{ k}\Omega$, $330\text{ }\Omega$)
- 4) Inductor (0.22 mH)
- 5) Antenna
- 6) capacitor (22 pF)
- 7) Transistor (BS47)
- 8) Voltage supply (9 V)



Working of circuit:

The FM transmitter circuit operates by generating a carrier signal at a specific frequency in the FM radio band. The audio signal captured by the microphone modulates the carrier signal, varying its frequency based on the sound wave's amplitude. This modulated signal is then transmitted through the antenna, which radiates it into the surrounding area.

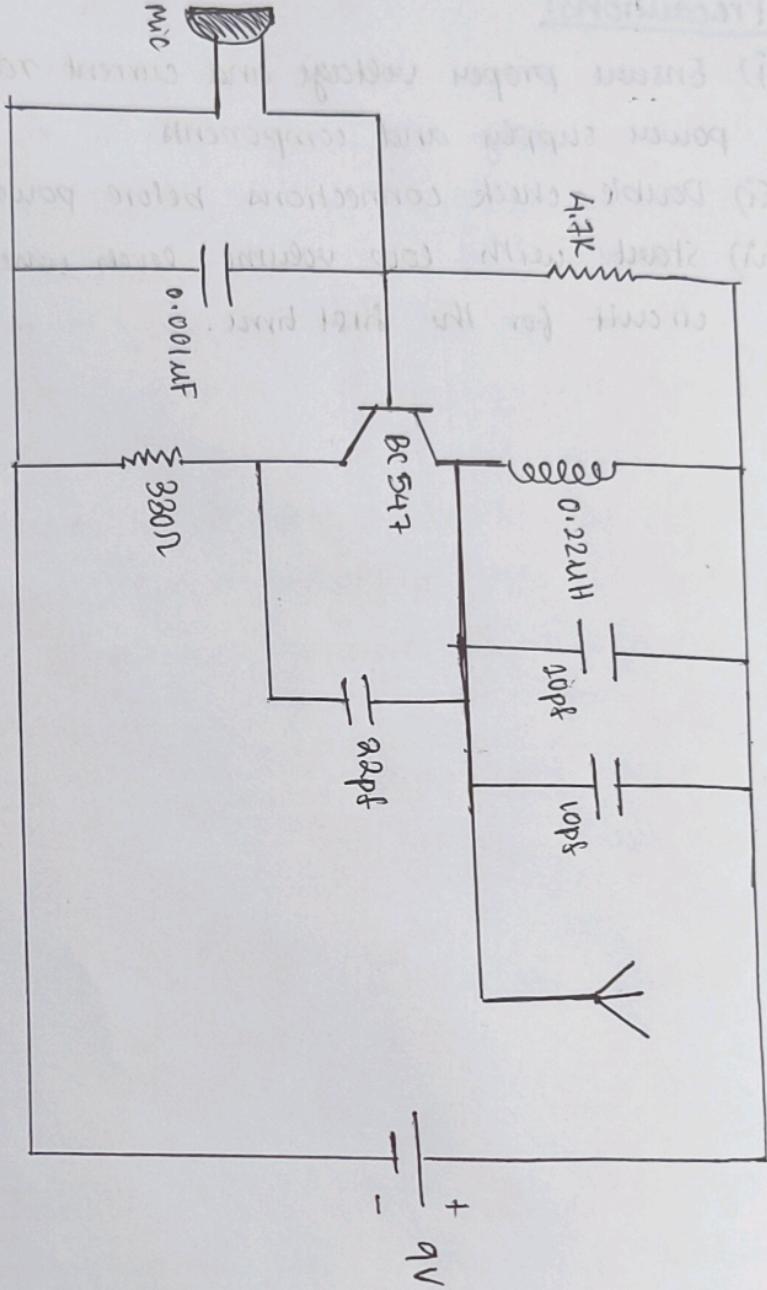Microphone: Called condenser mike also. It converts sound waves into electrical audio signals.





0.001 μF capacitor used / Bypass capacitor: Bypass

capacitor primarily deal with AC signals. They allow signals to pass through them with minimal opposition, while blocking DC signals. It also maintains a more stable bias voltage.

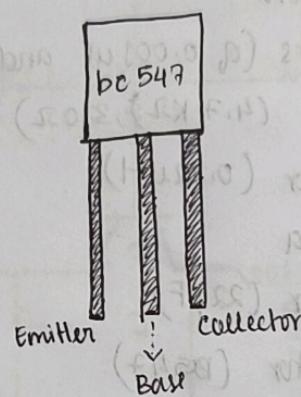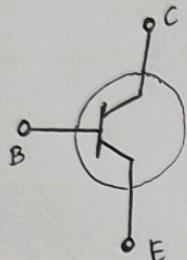4.7 kΩ resistor: 4.7 kΩ resistor is set the bias voltage of the transistor in oscillation section.

BC547 transistor: Used as the amplifier for the input signal coming from base.



Oscillator circuit (Transistor, Inductor, capacitors): Generates the carrier signal at the desired frequency. The transistor acts as an amplifier and oscillator, with the inductor and capacitors determining the oscillation frequency.

22 pF: Is the feedback circuit/network that helps control the gain and stability of the oscillator.

The feedback loop typically involves a portion of the amplified output signal from the transistor being fed back to its input (the base is most common configurations).

Antenna: Radiates the modulated FM signal wirelessly.

Procedure:

- 1) Connect the components as per the circuit diagram provided, ensuring proper connections and polarity.
- 2) Connect the microphone to the input of the circuit.
- 3) Apply the 9V power supply to the circuit.
- 4) Tune an FM radio to an empty frequency in the FM band.
- 5) Adjust the variable capacitor or inductor to fine-tune the output frequency of the transmitter.
- 6) Speak into the microphone to modulate the signal.
- 7) Tun the FM radio to receive the transmitted signal.

Observation:

- 1) You first need to set up your device to scan the frequency that is emitted by fm transmitter. It was "88.3 MHz" in our case.
- 2) Tap Test: As you tap the mic, you can identify which frequency corresponds to your fm transmitter.
- 3) As we play a song through the mic, you should be able to hear it.
- 4) Noise can be reduced as you change the orientation of mic.

Calculation:

The frequency to be emitted can be calculated as

$$f_{\text{emitted}} = f_{\text{carrier}} + \Delta(f).$$

where $f_{\text{carrier}} = \frac{1}{2\pi\sqrt{LC}}$ and $\Delta(f)$ is frequency

caused by modulation, which is proportional to the amplitude of audio signal. So our f_{carrier}
 $= 75.91 \text{ MHz}$

and found out $f_{\text{emitted}} = 97.7 \text{ MHz}$

Precaution:

- 1) Ensure proper connections and polarity to avoid short circuit.
- 2) Avoid interference with other electronic devices, radio signals.
- 3) Use appropriate safety measures when working with power sources.

Conclusion: